

Section 1: Circuit Symbols


Symbol	Name	Function
	Switch (open)	Enables current to be switched on or off.
	Cell	Pushes electrons around a complete circuit.
	Battery	Supplies electrical energy, consists of two or more cells.
	Diode	Allows current in one direction only.
	LED	Light emitting diode emits light when a current passes through it in the correct direction.
	Resistor	Limits the current in a circuit.
	Variable resistor	Allows current to be varied.
	Bulb	Emits light as a signal when a current passes through it.
	Fuse	Breaks the circuit if current exceeds a certain amount.
	Voltmeter	Measures potential difference (voltage).
	Ammeter	Measures electric current.
	Thermistor	Temperature dependent resistor. Has high resistance when temperature is low.
	LDR	A light dependent resistor. Has high resistance when levels of light are low.

Section 2: Key Terms

Electric current	Flow of electric charge . Units amperes, A
Potential difference	The potential difference (voltage) between two points in an electric circuit is the energy transferred (or the work done) when a coulomb of charge passes between the points. Units volt, V
Resistance	Resistance is caused by anything that opposes the flow of electric charge . Units ohm, Ω
Charge	Anything charged that is able to move within a circuit . Electrons or ions. Units are coulombs, C
Series	A circuit with only one route for charge to take . The different components are connected in a line, end to end.
Parallel	A circuit with more than one route for charge to take . Each component separately connected to the +ve and -ve terminals.

Section 3: The standard test circuit

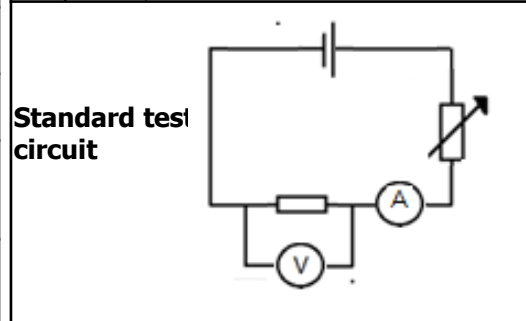The standard test circuit is used to test components and determine the resistance of a component. By measuring the current through and potential difference across the component, the resistance can then be calculated and IV graphs obtained.




The **Ammeter** must be in **series** and placed **anywhere** in the **circuit**.

The **voltmeter** must be placed in **parallel around the component** (so that it can compare the energy the charge has before and after passing through the component).

Section 4: Current-potential difference graphs

Increasing or decreasing the **potential difference** of the circuit will affect the current. Plotting current-potential difference results for different wires tells us about the resistance of these wires.


The **steeper the line, the lower the resistance** of the wire.

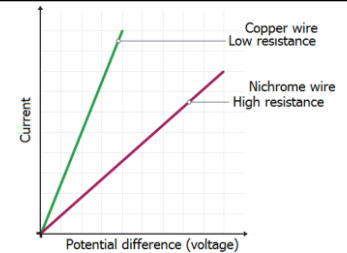

Section 5: Factors affecting resistance of a wire

Length of wire	The resistance of a wire is affected by length. Resistance of a long wire is greater than the resistance of a short wire because electrons collide with more metallic nuclei as they pass through.
Thickness of wire	The resistance of a thin wire is greater than the resistance of a thick wire because a thin wire has fewer electrons to carry the current.
Temperature	As temperature increases the metal nuclei begin to vibrate more. The electrons will have more chance of colliding and so resistance increases .

Electrical **current** is **NOT** the flow of electrons, it's the **flow of electric charge**, and as charge can be positive or negative then naturally **current** is in the **direction** of positive charge flow, and in the **opposite direction** to negative charge flow.

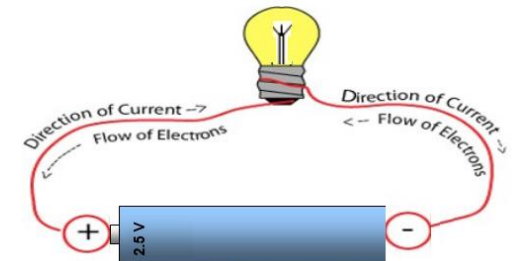

Section 6: V, I and R in Series and Parallel

Components connected in...	Current	Potential Difference	Resistance
<p>Series</p>	<p>The current is the same everywhere in the circuit and in every component.</p>	<p>The total potential difference of the power supply is shared between the components.</p>	<p>The total resistance is the sum of the individual resistances. $R_{\text{total}} = R_1 + R_2$ Adding more resistors increases resistance.</p> <p><u>Total resistance = 6 Ω</u></p>
<p>Parallel</p>	<p>The total current through the whole circuit is the sum of the currents through the separate components.</p>	<p>The potential difference across each component is the same.</p>	<p>The total resistance of two resistors is less than the resistance of the smallest individual resistor.</p> <p>The total resistance for this circuit is less than 2Ω (the resistance of the smallest resistor). Resistance decreases as more resistors are added.</p>

Section 7: IV Graphs

Graph	Example	Explanation
	<p>Ohmic conductor (Fixed resistor or wire)</p>	<p>Fixed Resistor or wires are Ohmic Conductors. Current and potential difference are directly proportional. Resistance is constant.</p>
	<p>Filament Lamp (bulb) non Ohmic conductors</p>	<p>Resistance of a filament lamp is not constant. As temperature increases, resistance increases. Ions within the lamp vibrate more, increasing collisions with electrons.</p>
	<p>Diode or LED</p>	<p>Diode/LED The current through a diode/LED flows in one direction only. The diode has a very high resistance in the reverse direction.</p>

Section 8: Equations to learn


Charge = current x time $Q = I \times t$	Charge flow - coulomb (C) Current - amperes (A) Time - seconds (s)
Potential difference = current x resistance $V = I \times R$	Potential difference - volts (V) Current - amperes (A) Resistance - ohms (Ω)
Energy transferred = charge x potential difference $E = Q \times V$	Energy = joules (J) Charge flow - coulomb (C) Potential difference - volts (V)

Section 9: Static electricity

Static electricity is all about charges which are **not free to move**. This causes them to build up in one place which leads to **sparks** or **shocks** when they finally do move.

Build up of static is caused by friction	When two insulating materials are rubbed together , electrons are scraped off one and dumped on the other. This leaves a positive static charge on one, and a negative static charge on the other.
Only electrons move	When electrons (negatively charged particles) move, ions form. Both positive and negative electrostatic charges form as a result.
Positive charges don't move	A positive charge is always caused by electrons being removed (so the positive charges don't move!)
Like charges repel	Two things with the same charge will repel each other.

Van de Graaff Generator

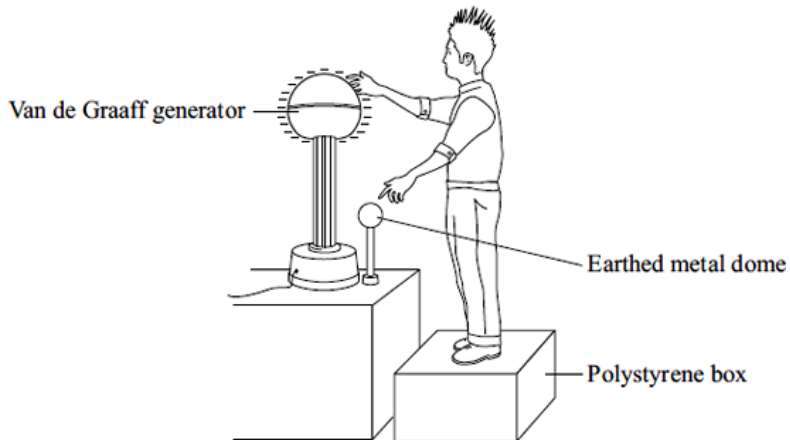

When the Van de Graaff generator is switched on, **each hair gains the same negative charge**. Similar **charges repel** so the students **hair stands on end**.

Examples of static electricity

- **Attracting dust:** many objects around a house are insulating materials and get easily charged. Dust particles are attracted to anything that's charged (TV screen, glass, plastic etc.)
- **Clinging clothes and crackles:** When synthetic clothes are dragged over each other (in tumble drier or over your head) electrons get scraped off leaving static electricity.
- **Bad hair days:** Static builds up on hair, each strand having the same charge, so they repel each other.

Section 10: Key Terms

Static electricity	It's the movement of electrons from one insulator to another. The insulator that loses electrons becomes positively charged and the insulator that gains the electrons becomes negatively charged
Insulator	An electrical insulator does not easily allow electricity to pass through it.
Earthing	Connecting a charged object to the ground using a conductor (e.g. copper wire) prevents build up of charge.

Section 11: Dangers

Lightning	Lightning is a sudden electrostatic discharge that usually occurs during a thunderstorm. This occurs between electrically charged regions of a cloud, between two clouds, or between a cloud and the ground.
Synthetic clothes	Static charge can build up on synthetic materials if they are rubbed against each other. The charge can eventually build up large enough to cause a spark, dangerous if close to flammable gases or fuel fumes.
Grain chutes, paper rollers, fuel pipes	Static can build up when grain shoots out of pipes/paper drags over rollers/fuel flows out of filler pipes. Can lead to a spark which might cause an explosion in dusty or fume-y places (like petrol station)
The solution to the problem	Earthing of objects prevents build up of static charge. Earthing cables can be attached to prevent sparks. Conducting soles in shoes prevent static electricity from building up hence preventing you getting a shock.

Section 12: Uses

Electrostatic paint sprayers	Used to paint bikes and cars providing a fine even coat.
Defibrillator	A shock from a defibrillator can restore normal heart rhythm. Consists of two paddles connected to a power supply which are placed on the patients chest. The charge passes through the paddles to the patient which makes the heart contract.